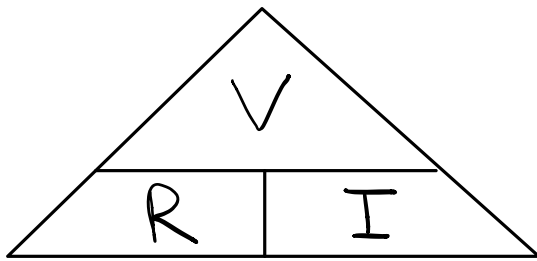


# Mechatronics / Electrical Signals

- DC (=direct current) motors are more complex and less efficient than AC (=alternate current) motors
  - ↳ - DC easier to manipulate / easier math
  - integration is easier/cheaper (e.g. batteries produce DC current)
- Circuit analysis: usually voltage is given → calculate current




$$V = R \cdot I$$

$$R = V / I$$


$$I = V / R$$
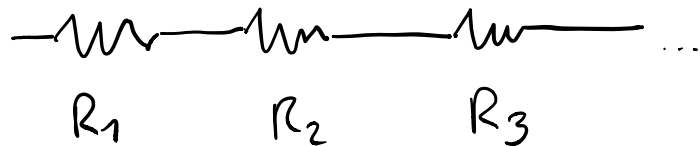
## OHM'S LAW

Resistors in series:  $R_T = R_1 + R_2 + R_3 \dots$



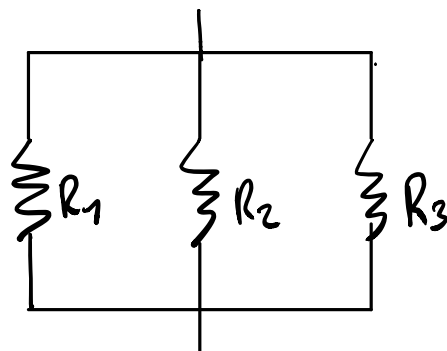
Resistors in parallel:  $\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$



Voltages in series:  $V_T = V_1 + V_2 + V_3 \dots$

Current in series:


$$I_T = I_1 = I_2 = I_3$$

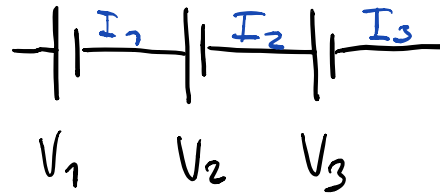

Voltages in parallel:  $V_T = V_1 = V_2 = V_3$

Current in parallel:

$$I_T = I_1 + I_2 + I_3$$

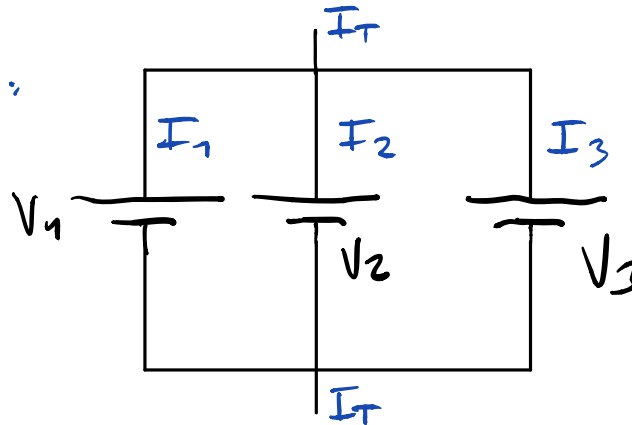

Kirchoff's Laws:

- algebraic sum of currents meeting at one point is zero
- direct sum of voltages in closed loop is zero

When analyzing complex networks, choose direction of current

→ voltage rise is positive, voltage drop is negative